

# *SEE 3243/4243*

## *Digital System*

### **Week 5: Arithmetic Circuits Part 1**

- Binary Number Representation
  - Sign & Magnitude
  - Ones Complement
  - Twos Complement
- Networks for Binary Addition
  - Half Adder
  - Full Adder
  - Ripple Adder
  - Subtractor



## *Motivation*

- Arithmetic circuits are excellent examples of comb. logic design
  
- Time vs. Space Trade-offs
  - Doing things fast requires more logic and thus more space
  - Example: carry lookahead logic
  
- Arithmetic Logic Units
  - Critical component of processor datapath

## *Unsigned Integers*

- Smallest representable value: bit
- Bit groups represent information
- Number of bits determine max. combinations of information
- $N$  bits =  $2^N$  values

Number of Bits	Number of values	Machine
4	16	Intel 4004
8	256	8080, 6800
16	65536	PDP11, 8086, 68000
32	$\sim 4 \times 10^9$	IBM 370, 68020, VAX11/780, IEEE single
48	$1 \times 10^{14}$	Unisys
64	$1.8 \times 10^{19}$	Cray, IEEE double

## *Unsigned Integers*

- Value for the bit pattern:

$$V_{unsigned} = \sum_{i=0}^{N-1} b_i \times 2^i$$

- Example:

$$10110_2 = 1 \times 2^4 + 0 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 0 \times 2^0 = 22_{10}$$

- How many numbers can 8-bit represent?
- For N bits, range of values:  
0 up to  $2^N - 1$




## *Representation of Negative Numbers*

- Representation of positive numbers same in most systems
- Major differences are in how negative numbers are represented
- Three major schemes:
  - sign and magnitude
  - ones complement
  - twos complement
- Assumptions:
  - 4-bit machine word
  - 16 different values can be represented
  - roughly half are positive, half are negative

## *Sign and Magnitude*

- Easiest to understand
- Leftmost bit (MSB) is sign bit
  - 0 means positive
  - 1 means negative
- $+18 = 00010010$
- $-18 = 10010010$
- All digit strings with leftmost digit = 0 are positive numbers
- Positive numbers are represented like natural binary numbers
- For a negative number, the magnitude of that number is equal to whatever you get by interpreting all the bits other than the sign bit in the natural way

# Sign and Magnitude

 

- Example for N=4:
  - High order bit is sign: 0 = positive (or zero), 1 = negative
  - Three low order bits is the magnitude: 0 (000) thru 7 (111)
  - Number range for n bits =  $\pm(2^{n-1}-1)$
  - Two representations for 0 (0000 and 1000)



## *Sign-and-Magnitude Problems*

- Easy for humans to understand, but may not be the best for machine operation efficiency
- Cumbersome addition/subtraction
- Must compare magnitudes to determine sign of result
- Need to check both sign and magnitude in arithmetic
- Two representations of zero (+0 and -0)



## *Ones' Complement Representation*

- Ones' complement defined as

$$\overline{N} = (2^n - 1) - N$$

- In ones' complement we get the negation of a number by flipping all the bits
- The name ones' complement comes from the fact that we could also get the negation of a number by subtracting each bit from 1
- Complement of a complement generates original number

# Ones' Complement Representation

$$\overline{N} = (2^n - 1) - N$$

- Ones' complement of +7
  - Since  $n=4$ ,  $(2^n - 1) = 1111$

$2^n - 1$	1	1	1	1	
N	0	1	1	1	(+7)
$\overline{N}$	1	0	0	0	(-7)

- Ones' complement of -7

$2^n - 1$	1	1	1	1	
N	1	0	0	0	(-7)
$\overline{N}$	0	1	1	1	(+7)



Shortcut method:

simply compute bitwise complement

1001 -> 0110

# Ones' Complement Representation

$$\overline{N} = (2^n - 1) - N$$

  

- Some complexities in addition
- Subtraction implemented by addition & 1's complement
- Still two representations of 0! This causes some problems

## *Two's Complement*



- Two's complement defined as

$$N^* = 2^n - N \text{ for } N \neq 0$$
$$0 \text{ for } N = 0$$

- Exception is so result will always have n bits
- Two's complement is just a 1 added to 1's complement
- Complement of a complement generates original number
  
# Twos Complement Representation

*like 1's comp  
except shifted  
one position  
clockwise*



- Only one representation for 0
- One more negative number than positive number

# Two's Complement Representation

$$N^* = 2^n - N$$

- Two's complement of +7

$2^n$	1 0000	
N	0111	(+7)
$N^*$	1001	(-7)

- Two's complement of -7

$2^n$	1 0000	
N	1001	(-7)
$N^*$	0111	(+7)

Shortcut method:

Twos complement = bitwise complement + 1

0111 -> 1000 + 1 -> 1001 (representation of -7)

1001 -> 0110 + 1 -> 0111 (representation of 7)

# Finding 2's Complement

Complement  
remaining bits

Copy all bits  
to first 1

0	1	0	1	1	0	0	0
1	0	1	0	1	0	0	0

2's complement

Start here

**Table 2-6** Decimal and 4-bit numbers.

<i>Decimal</i>	<i>Two's Complement</i>	<i>Ones' Complement</i>	<i>Signed Magnitude</i>
-8	1000	—	—
-7	1001	1000	1111
-6	1010	1001	1110
-5	1011	1010	1101
-4	1100	1011	1100
-3	1101	1100	1011
-2	1110	1101	1010
-1	1111	1110	1001
0	0000	1111 or 0000	1000 or 0000
1	0001	0001	0001
2	0010	0010	0010
3	0011	0011	0011
4	0100	0100	0100
5	0101	0101	0101
6	0110	0110	0110
7	0111	0111	0111



## Range of Numbers

- 4-bit 2s complement

- $+7 = 0111 = 2^3 - 1$

- $-8 = 1000 = -2^3$

- 8 bit 2s complement

- $+127 = 01111111 = 2^7 - 1$

- $-128 = 10000000 = -2^7$

- 16 bit 2s complement

- $+32767 = 01111111 11111111 = 2^{15} - 1$

- $-32768 = 100000000 00000000 = -2^{15}$

- N bit 2s complement

- $01111111..11111111 = 2^{N-1} - 1$  (largest positive)

- $100000000..00000000 = -2^{N-1}$  (largest negative)

## *Conversion Between Lengths, e.g. 8 → 16*

- **Positive number: add leading zeros**
  - +18 =                   00010010
  - +18 = 00000000 00010010
- **Negative numbers: add leading ones**
  - -18 =                   11101110
  - -18 = 11111111 11101110
- **i.e. pack with msb (sign bit)**

called “**sign extension**”



## *Addition and Subtraction*

- $a - b = ?$
- Normal binary addition
- Monitor sign bit of result for overflow
  
- Take negation of  $b$  and add to  $a$ 
  - i.e.  $a - b = a + (-b)$
- So we only need **addition** and **complement** circuits

## Addition and Subtraction : Ones Complement

4	0100	-4	1011
<u>+ 3</u>	<u>0011</u>	<u>+ (-3)</u>	<u>1100</u>
7	0111	-7	10111
	End around carry		1
			1000

4	0100	-4	1011
<u>- 3</u>	<u>1100</u>	<u>+ 3</u>	<u>0011</u>
1	10000	-1	1110
End around carry	1		
	0001		

# Addition and Subtraction : Twos Complement

$\begin{array}{r} 4 \quad 0100 \\ + 3 \quad 0011 \\ \hline 7 \quad 0111 \end{array}$	$\begin{array}{r} -4 \quad 1100 \\ + (-3) \quad 1101 \\ \hline -7 \quad 11001 \end{array}$	<p>If carry-in to sign = carry-out then ignore carry</p>
$\begin{array}{r} 4 \quad 0100 \\ - 3 \quad 1101 \\ \hline 1 \quad 10001 \end{array}$	$\begin{array}{r} -4 \quad 1100 \\ + 3 \quad 0011 \\ \hline -1 \quad 1111 \end{array}$	<p>If carry-in to sign = carry-out then ignore carry</p>

- Simpler addition scheme makes twos complement the most common choice for integer number systems within digital systems





## *Addition and Subtraction : Twos Complement*

- Why can the carry-out be ignored?
- Add 2's complement of N to M
  - This is  $M - N = M + N^*$
- If  $M \geq N$ , will generate carry
  - $M + N^* = M + (2^n - N) = M - N + 2^n$
  - Discard carry: just like subtracting  $2^n$
  - Result is positive  $M - N$
- If  $M < N$ , no carry
  
# Overflow Conditions

- Add two positive numbers to get a negative number
- or two negative numbers to get a positive number



# Twos Complement Overflow

	Expected	0 1 1 1	Actual
	+5	0 1 0 1	
+	+3	0 0 1 1	
<hr/>			
	+8	1 0 0 0	-8

Overflow

	Expected	1 0 0 0	Actual
	-7	1 0 0 1	
+	-2	1 1 1 0	
<hr/>			
	-9	0 1 1 1	+7

Overflow

	Expected	0 0 0 0	Actual
	+5	0 1 0 1	
+	+2	0 0 1 0	
<hr/>			
	+7	0 1 1 1	+7

No Overflow

	Expected	1 1 1 1	Actual
	-3	1 1 0 1	
+	-5	1 0 1 1	
<hr/>			
	-8	1 0 0 0	+8


No Overflow

Overflow when carry in to sign does not equal carry out


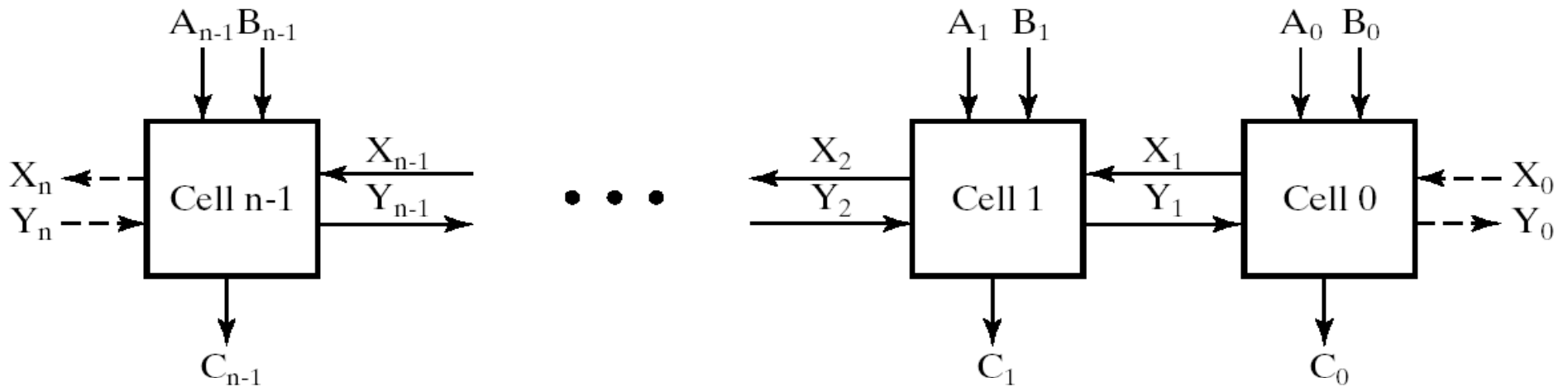
## Iterative Circuit

- Like a hierarchy, except functional blocks per bit



- Adders are a great example of this type of design
- Design 1-bit circuit, then expand
- Look at
  - Half adder – 2-bit adder, no carry in
    - Inputs are bits to be added
    - Outputs: result and possible carry
  - Full adder – includes carry in, really a 3-bit adder

# Half Adder

- Simplest adder block is “half adder”
  - Not very useful by itself


X	Y	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

X	0	1
Y	0	0
1	0	1

Carry = A B

X	0	1
Y	0	1
1	1	0

Sum = A' B + A B'  
= A ⊕ B

 

Half-adder Schematic

## Full Adders

- Basic building block is full adder
- Many full-adders are combined to add more than 1 bits
- Truth table:

<b>X</b>	<b>Y</b>	<b>C<sub>in</sub></b>	<b>C<sub>out</sub></b>	<b>S</b>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

# Full Adder

		XY			
	$C_{in}$	00	01	11	10
0		0	1	0	1
1		1	0	1	0

$$S = X \oplus Y \oplus C_{in}$$




		XY			
	$C_{in}$	00	01	11	10
0		0	0	1	0
1		0	1	1	1

$$C_{out} = XY + XC_{in} + YC_{in}$$

$$= XY + (X + Y)C_{in}$$


- In a multi-stage adder:
  - Variable  $i$  indicates stage number.
  - $C_{in}$  is carry to  $i$ -th stage, also known as  $C_i$
  - $C_{out}$  is carry to next stage, also known as  $C_{i+1}$
   
# Full-adder circuit: Straightforward Approach


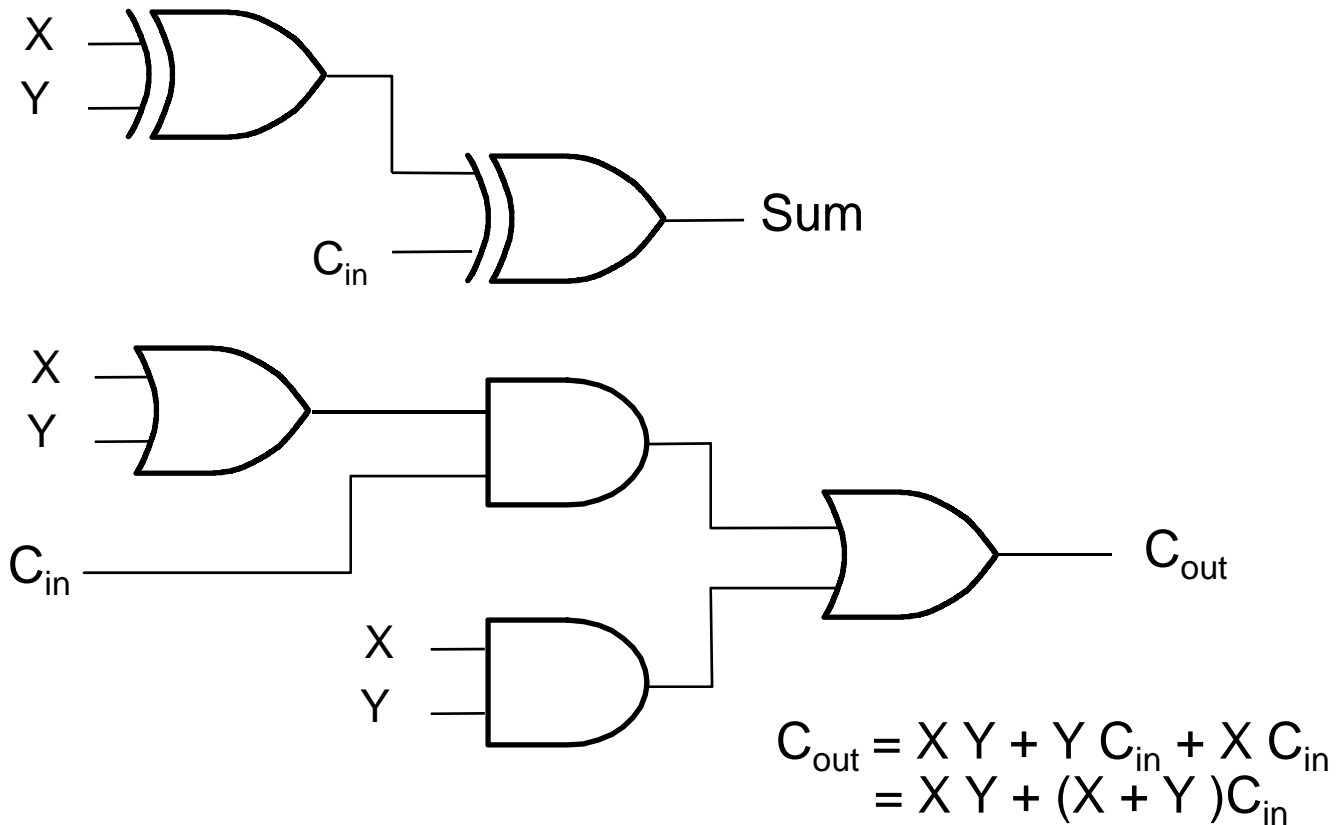
## Full Adder: Alternative Implementation

- Cost: 6 Gates, max. 2 inputs per gate, 3 levels of logic
- Advantage: All gates of 2-input type, easier to do VLSI layout



## Implementation with Two Half Adders (and an OR)

Cost: 5 Gates, 3 levels of logic


 


Fig. 3-27 Logic Diagram of Full Adder


# Ripple-Carry Adder

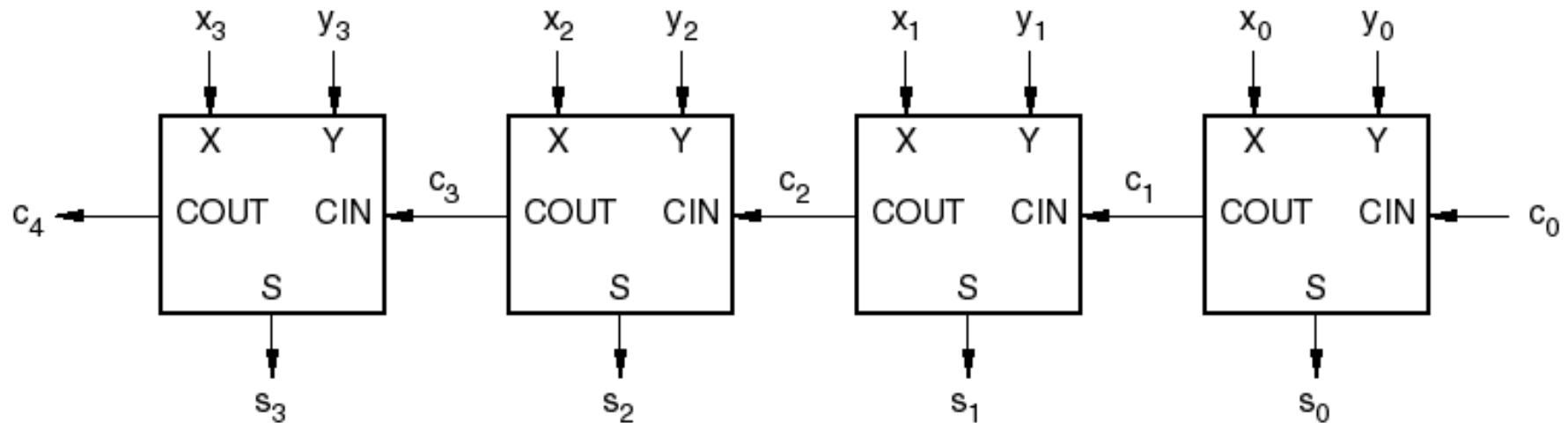

- Straightforward – connect full adders
- Carry-out to carry-in chain
  - $C_0$  in case this is part of larger chain, maybe just set to zero
- Speed limited by carry chain
- Faster adders eliminate or limit carry chain
  - 2-level AND-OR logic  $\implies 2^n$  product terms
  - 3 or 4 levels of logic, carry lookahead



# Overflow Detection

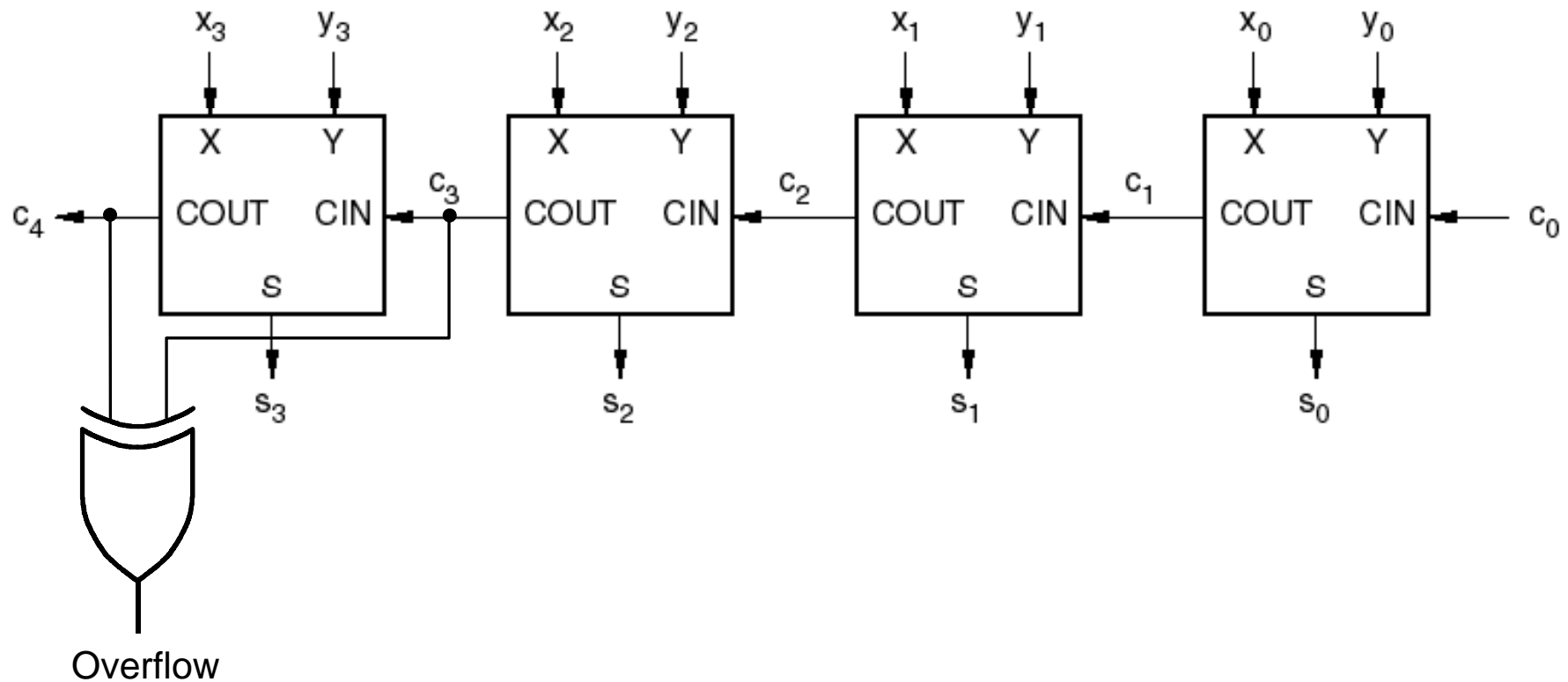

- If  $Overflow = 1$ , then overflow condition occurs. The output should not be used, i.e. the output is wrong.
- Condition is that either  $C_{n-1}$  or  $C_n$  is high, but not both ( $n = \#stages$ )

# Half Subtractor Circuit


X	Y	B	D
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

Difference

$$D = X'Y + XY' = X \oplus Y$$


Borrow

$$B = X'Y$$

 


# Full Subtractor Circuit

X	Y	B <sub>in</sub>	B <sub>out</sub>	D
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

 


Difference  
 $D = X \oplus Y \oplus B_{in}$

 Borrow out  
 $B_{out} = X'Y + X'B_{in} + YB_{in}$




# Multi-Stage Full Subtractor

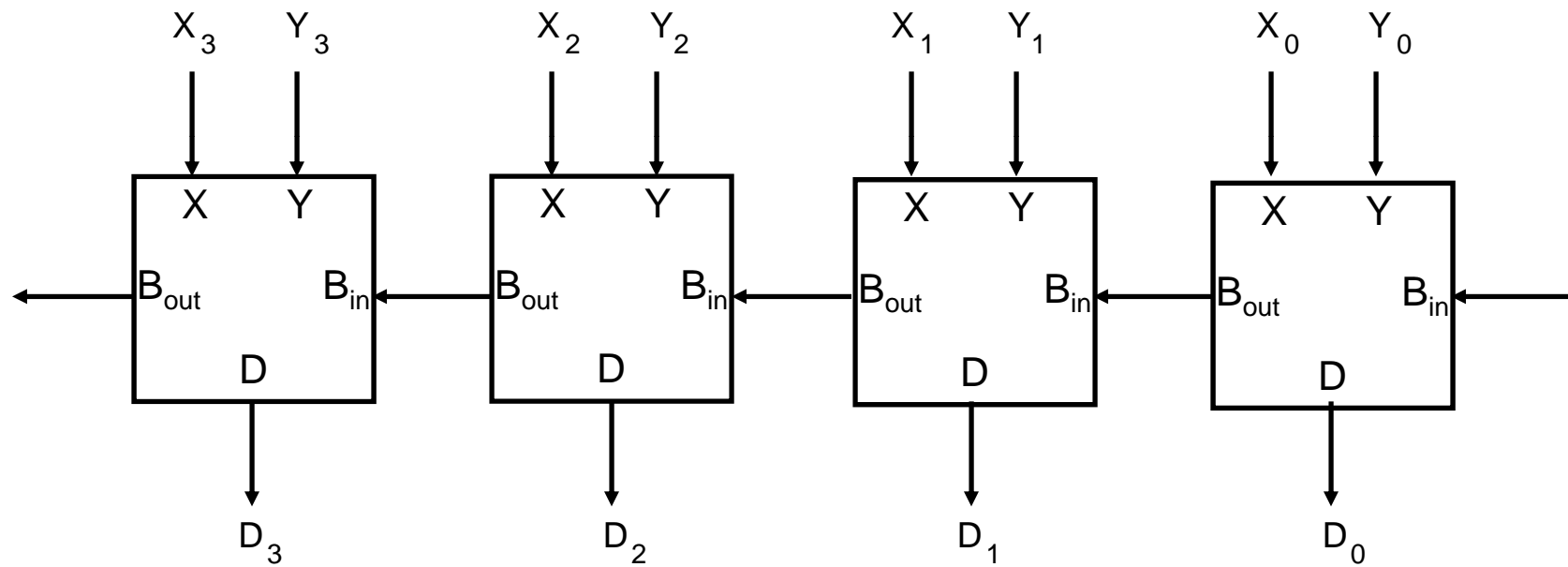

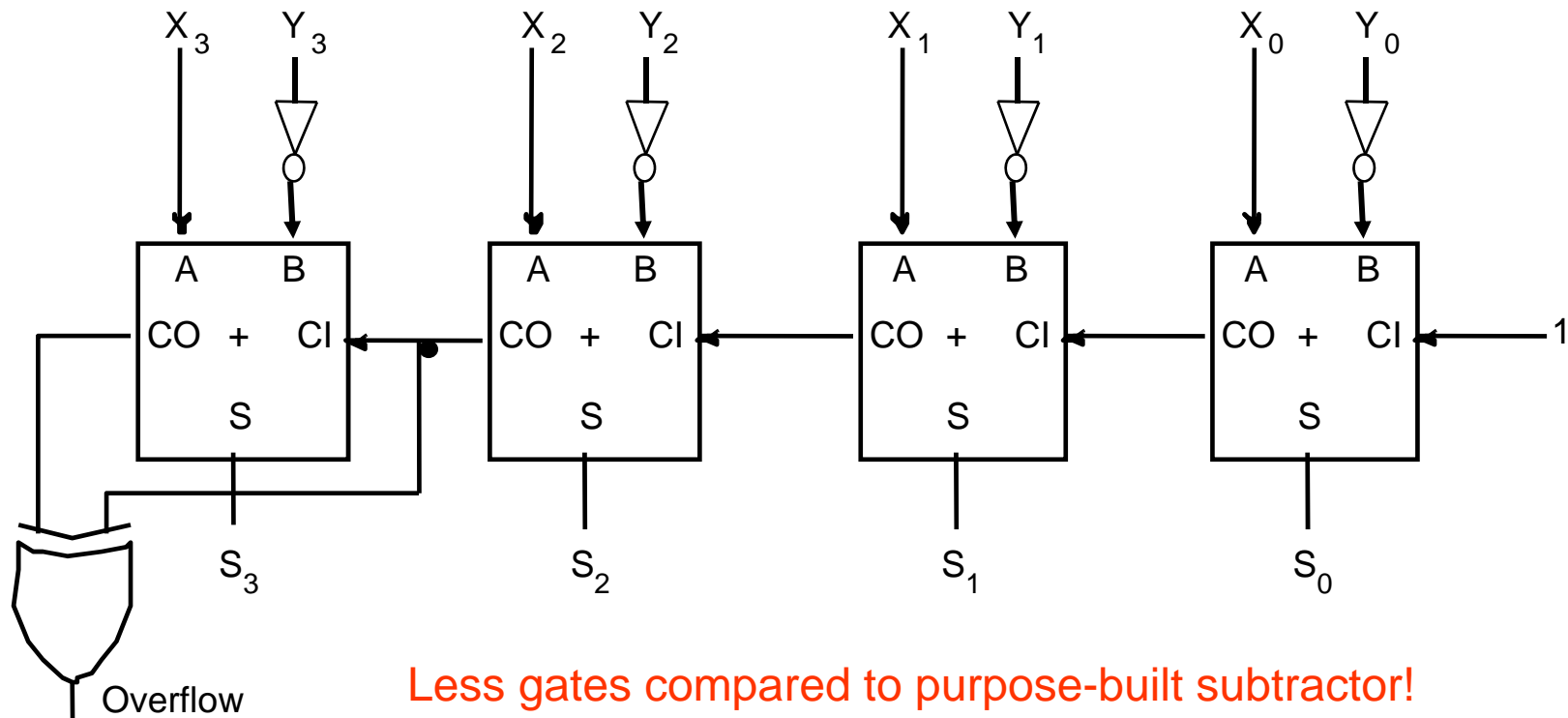
# Subtraction Using Adders

- Subtraction is the same as addition of the two's complement.
- The two's complement is the bit-by-bit complement plus 1.
- Therefore,  $X - Y = X + Y' + 1$ .
  - Complement Y inputs to adder, set  $C_1$  to 1.



Less gates compared to purpose-built subtractor!

# Adder/Subtractor

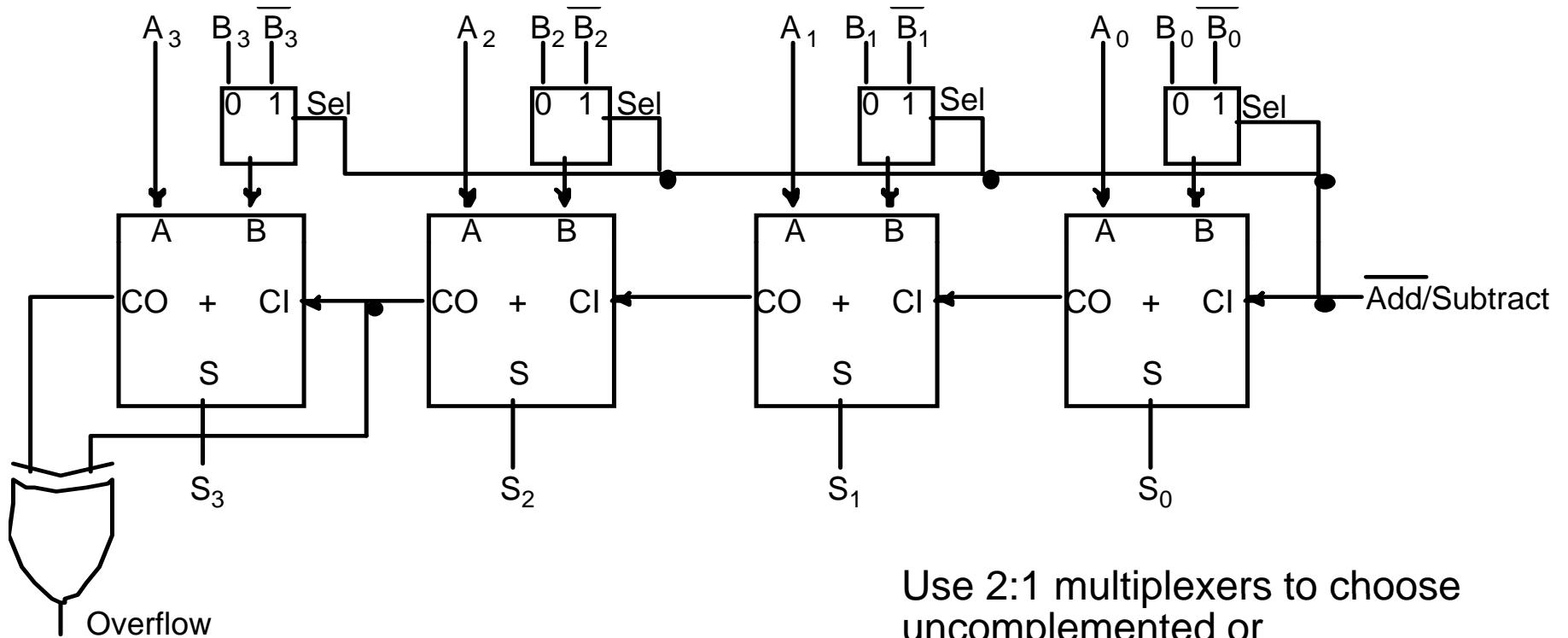

Use 2:1 multiplexers to choose uncomplemented or complemented inputs

Remember,  $A - B = A + (-B) = A + \overline{B} + 1$   
 So when Add/Sub = 0,  $S = A + B$   
 When Add/Sub = 1,  $S = A + \overline{B} + 1 = A - B$

# Alternative Design

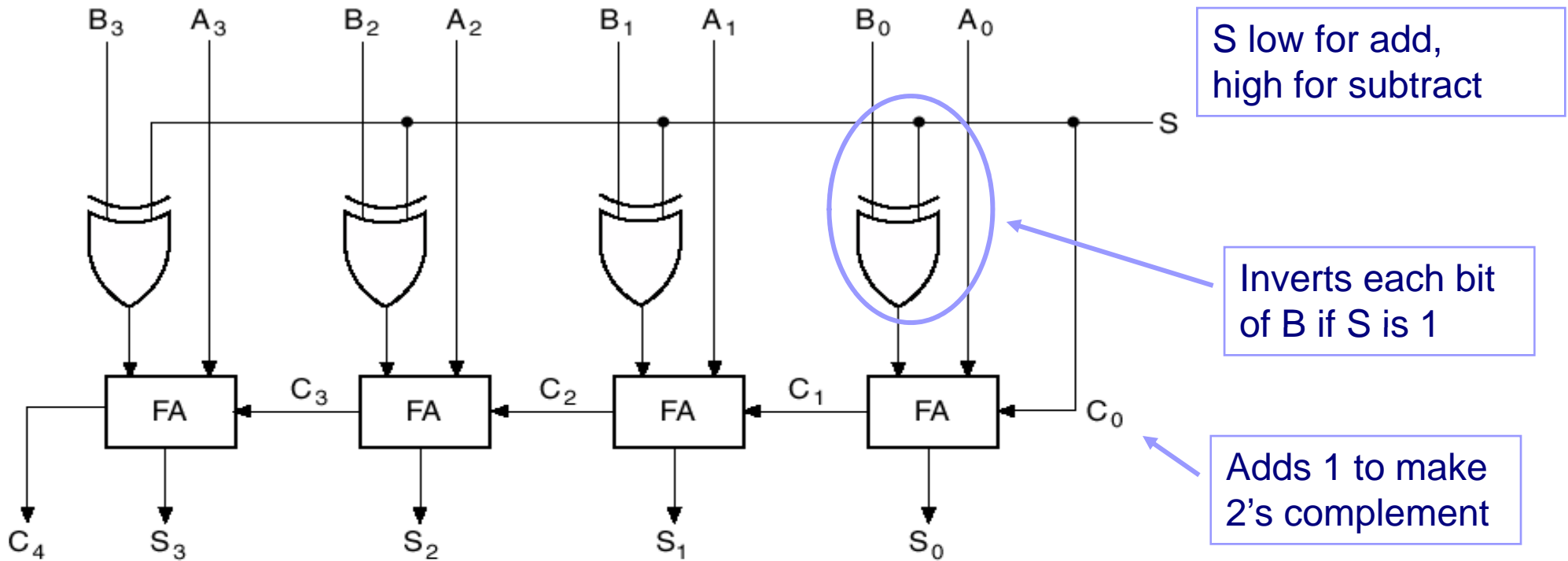


Fig. 3-31 Adder-Subtractor Circuit

- Output is 2's complement if  $B > A$



## *Exercise*

- Do Q5.2, Q5.7 Katz & Borriello textbook