

# *SEE 3243/4243*

## *Advanced FSM Implementation*

*Week 12*

- *Using PLA, ROM & counters for implementation*



## *State machine design*


- Construct state/output table
- Minimize number of states (optional)
- Assign state variables
- Choose flip-flop type (d or j-k)
- Construct excitation table
- Derive excitation equations
- Derive output equations
- Draw logic diagram




## *Implementation Strategies*

- Discrete logic
- Design with structured Logic
  - Counters
  - Shift Register
  - ROMs
- Programmable logic
  - PALs
  - FGPAs: Altera, Actel, Xilinx

# FSM Design with Structured Logic

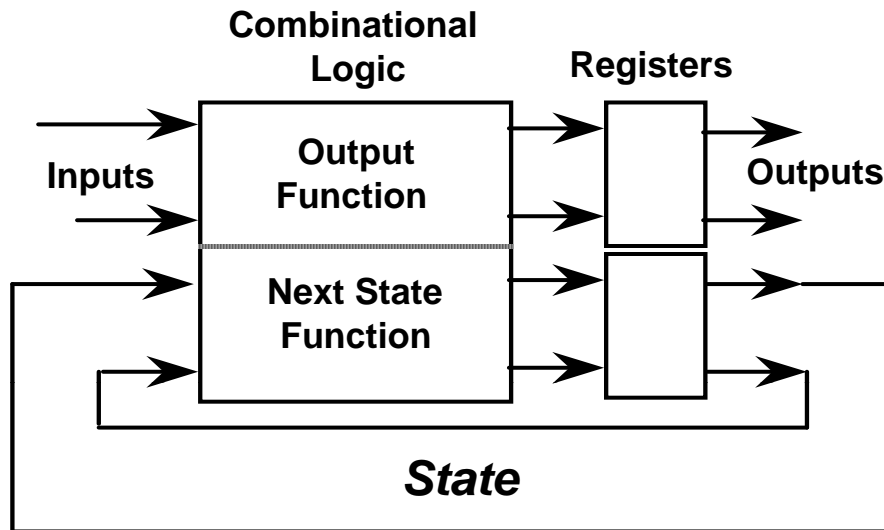

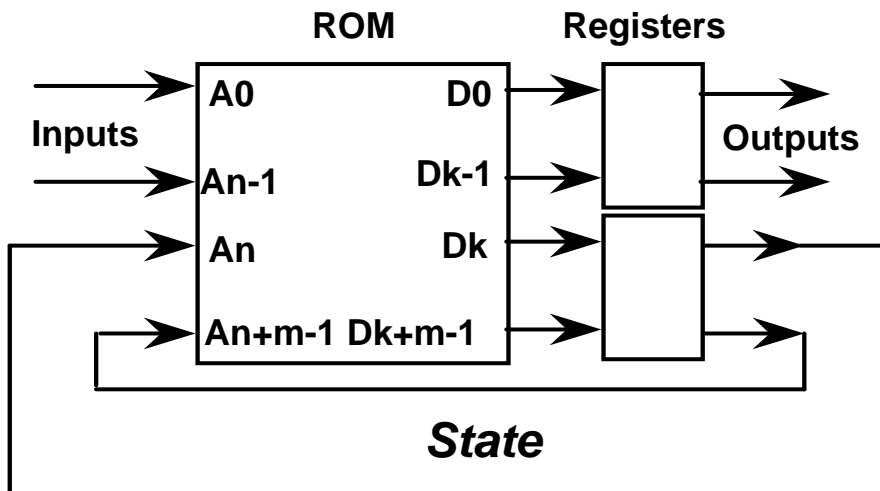Block Diagram for Synchronous Mealy Machine





ROM-based Realization

- Inputs & Current State form the address
- ROM data bits form the Outputs & Next State

# General structure of a clocked sequential network realization using a PLD and clocked *D* flip-flops.

Figure 7.31

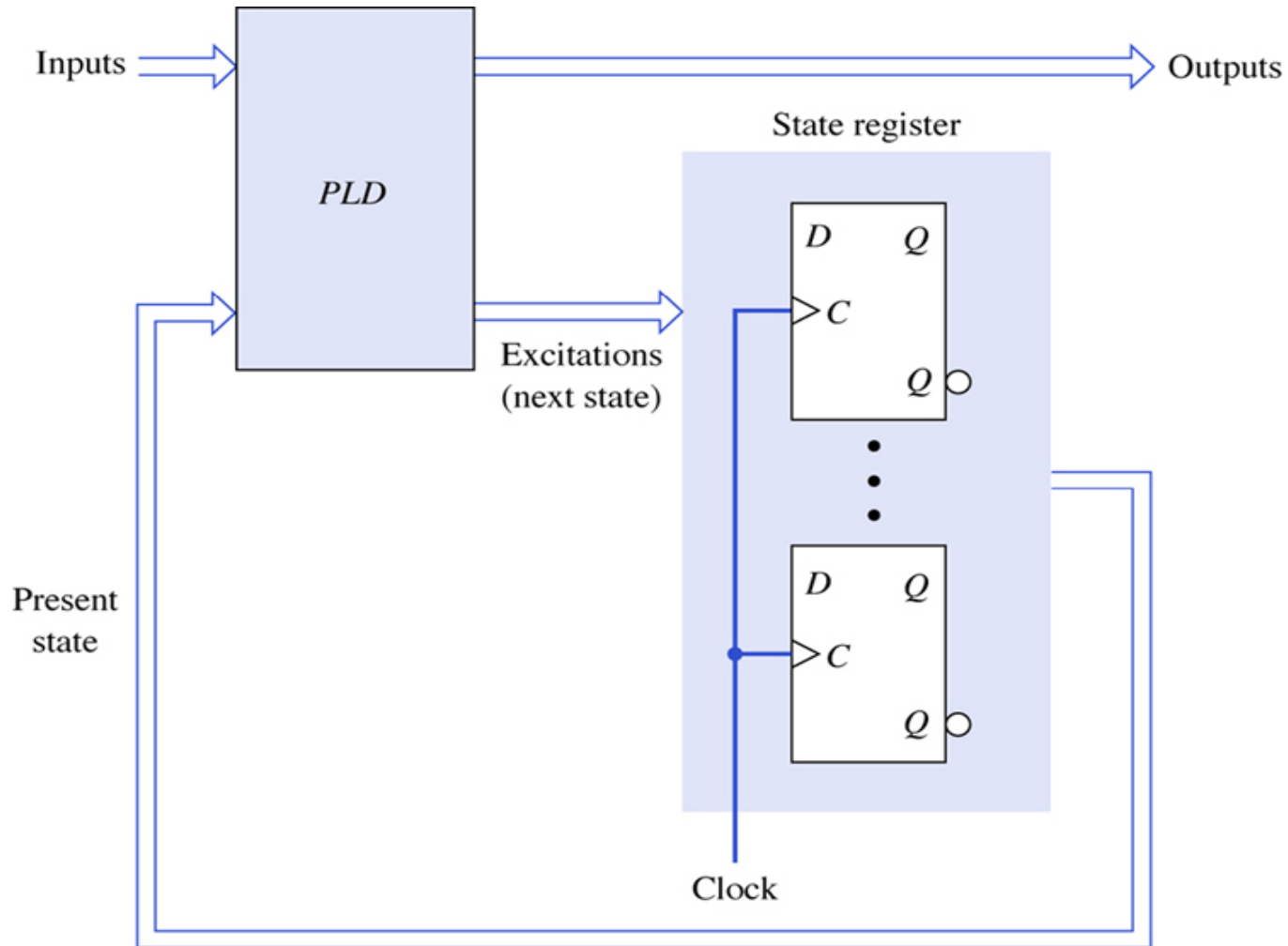

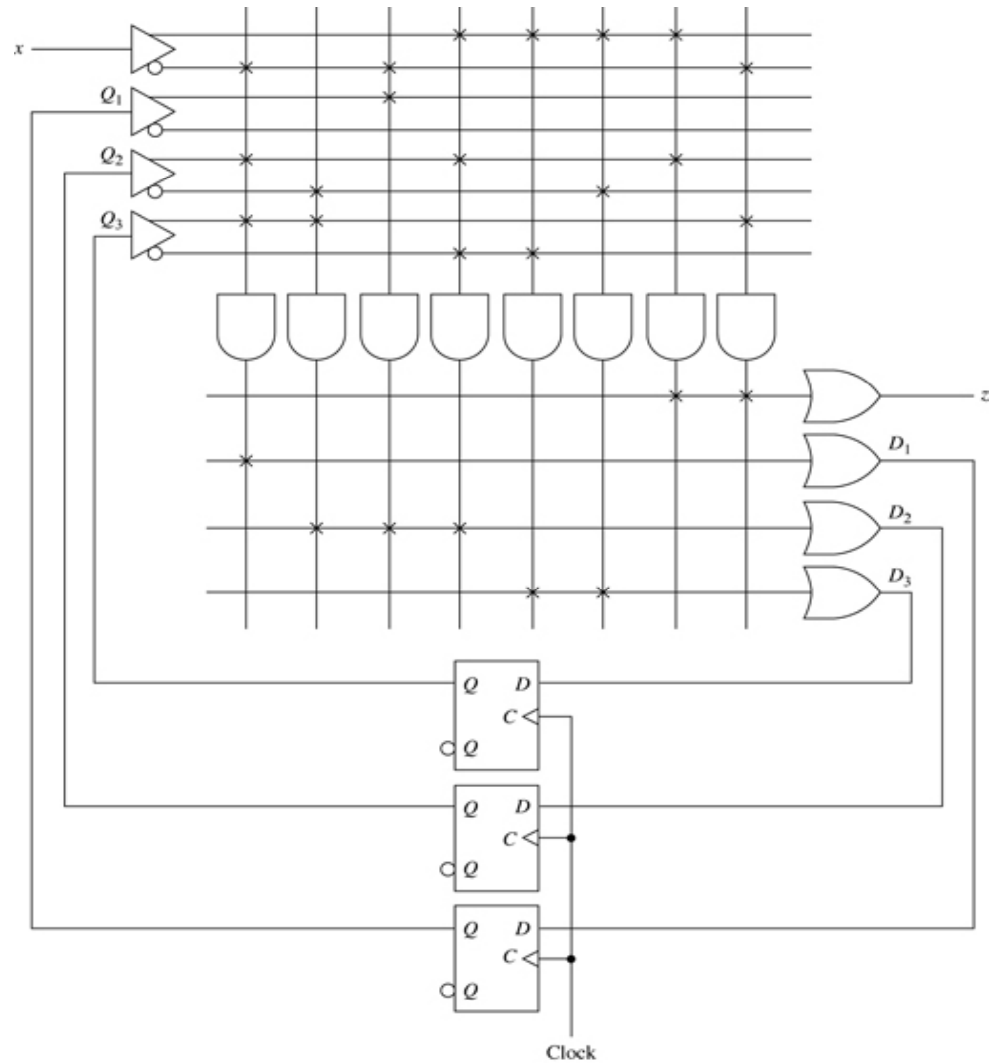

A clocked synchronous sequential network realization using a PLA and clocked  $D$  flip-flops.

# *BCD to Excess 3 Serial Converter*

## *ROM-based Design*

Example: BCD to Excess 3 Serial Converter

### *Conversion Process*

Bits are presented in bit serial fashion starting with the least significant bit


Single input X, single output Z

BCD	Excess 3 Code
0000	0011
0001	0100
0010	0101
0011	0110
0100	0111
0101	1000
0110	1001
0111	1010
1000	1011
1001	1100

# BCD to Excess 3 Serial Converter

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
S0	S1	S2	1	0
S1	S3	S4	1	0
S2	S4	S4	0	1
S3	S5	S5	0	1
S4	S5	S6	1	0
S5	S0	S0	0	1
S6	S0	--	1	--

State Transition Table

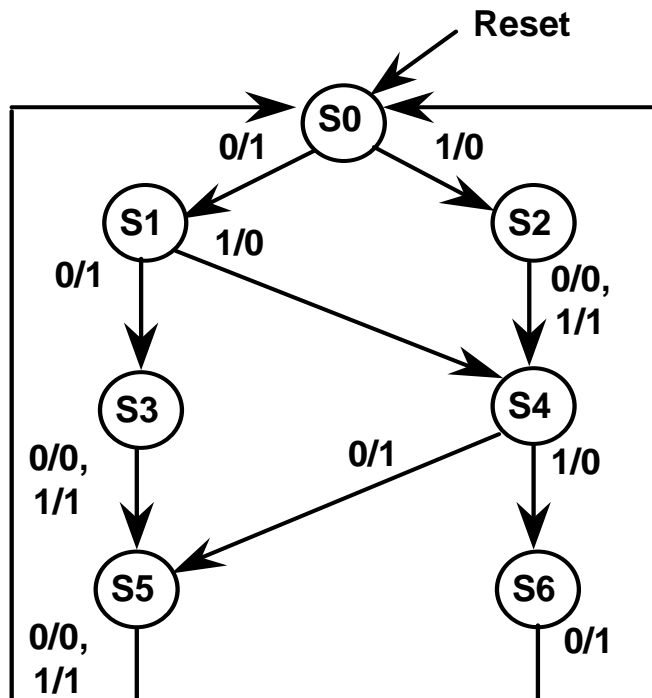

Derived State Diagram




# BCD to Excess 3 Serial Converter

ROM-based Implementation

ROM Address				ROM Outputs			
A3	A2	A1	A0	D3	D2	D1	D0
0	0	0	0	1	0	0	1
0	0	0	1	1	0	1	1
0	0	1	0	0	1	0	0
0	0	1	1	0	1	0	1
0	1	0	0	1	1	0	1
0	1	0	1	0	0	0	0
0	1	1	0	1	0	0	0
0	1	1	1	X	X	X	X
1	0	0	0	0	0	1	0
1	0	0	1	0	1	0	0
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	1
1	1	0	0	0	1	1	0
1	1	0	1	1	0	0	0
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

Truth Table/ROM I/Os

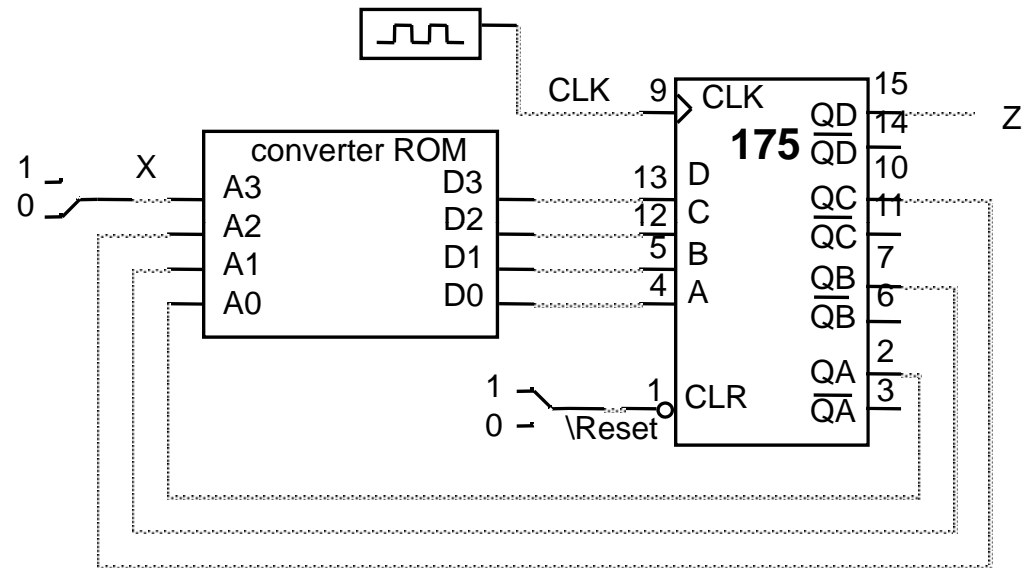


Circuit Level Realization  
74175 = 4 x positive edge triggered D FFs

In ROM-based designs, no need to consider state assignment
 
# BCD to Excess 3 Serial Converter

LSB

Timing Behavior for input strings 0 0 0 0 (0) and 1 1 1 0 (7)





# *Implementation Strategies*

**PLA-based Design**  
***BCD to Excess 3 Converter***

**S0 = 000**

**S1 = 001**

**S2 = 011**

**S3 = 110**

**S4 = 100**

**S5 = 111**

**S6 = 101**

# Implementation Strategies


## BCD to Excess 3 Converter

$$D2 = \overline{Q2} \cdot Q0 + Q2 \cdot \overline{Q0}$$

$$D1 = \overline{X} \cdot \overline{Q2} \cdot \overline{Q1} \cdot Q0 + X \cdot \overline{Q2} \cdot \overline{Q0} + \overline{X} \cdot Q2 \cdot \overline{Q0} + Q1 \cdot \overline{Q0}$$

$$D0 = \overline{Q0}$$
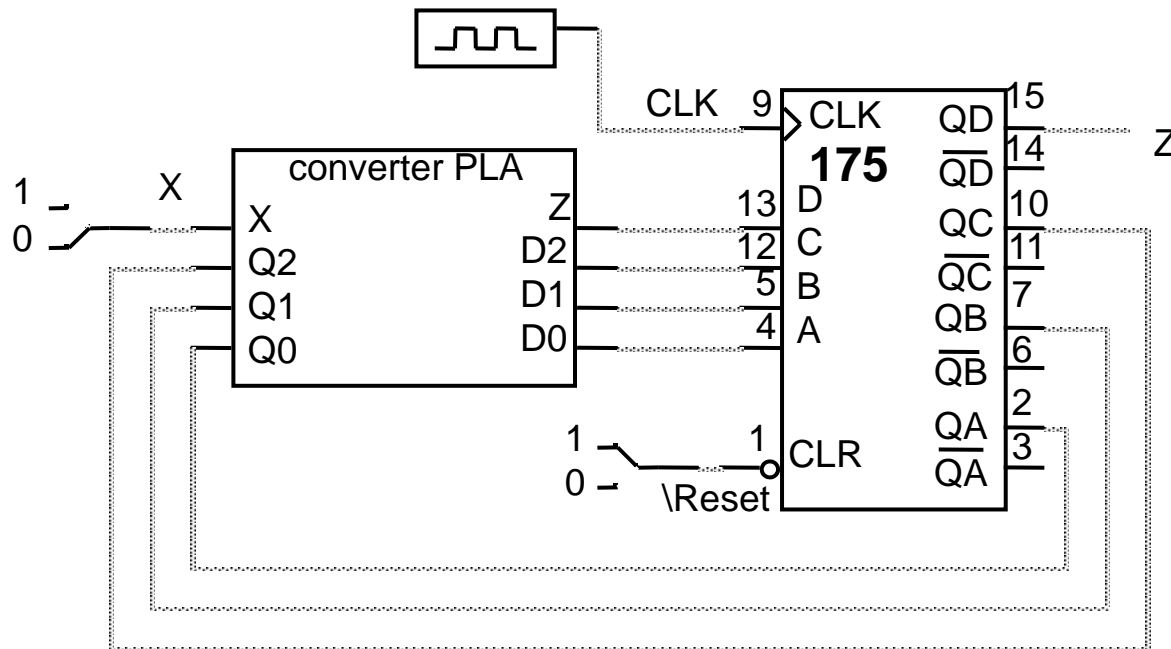
$$Z = X \cdot Q1 + \overline{X} \cdot \overline{Q1}$$



# Implementation Strategies

## BCD to Excess 3 Serial Converter


10H8 PAL: 10 inputs, 8 outputs, 2 product terms per OR gate

$$D1 = D11 + D12$$



$$D11 = \overline{X} \cdot \overline{Q2} \cdot \overline{Q1} \cdot Q0 + X \cdot \overline{Q2} \cdot \overline{Q0}$$

$$D12 = \overline{X} \cdot Q2 \cdot \overline{Q0} + Q1 \cdot \overline{Q0}$$

 - 0.  $\overline{Q2} \cdot Q0$
- 1.  $Q2 \cdot \overline{Q0}$
- 8.  $\overline{X} \cdot \overline{Q2} \cdot \overline{Q1} \cdot Q0$
- 9.  $X \cdot \overline{Q2} \cdot \overline{Q0}$
- 16.  $\overline{X} \cdot Q2 \cdot \overline{Q0}$
- 17.  $Q1 \cdot \overline{Q0}$
- 24. D11
- 25. D12
- 32.  $Q0$
- 33. not used
- 40.  $X \cdot Q1$
- 41.  $\overline{X} \cdot Q1$



# BCD to Excess 3 Serial Converter

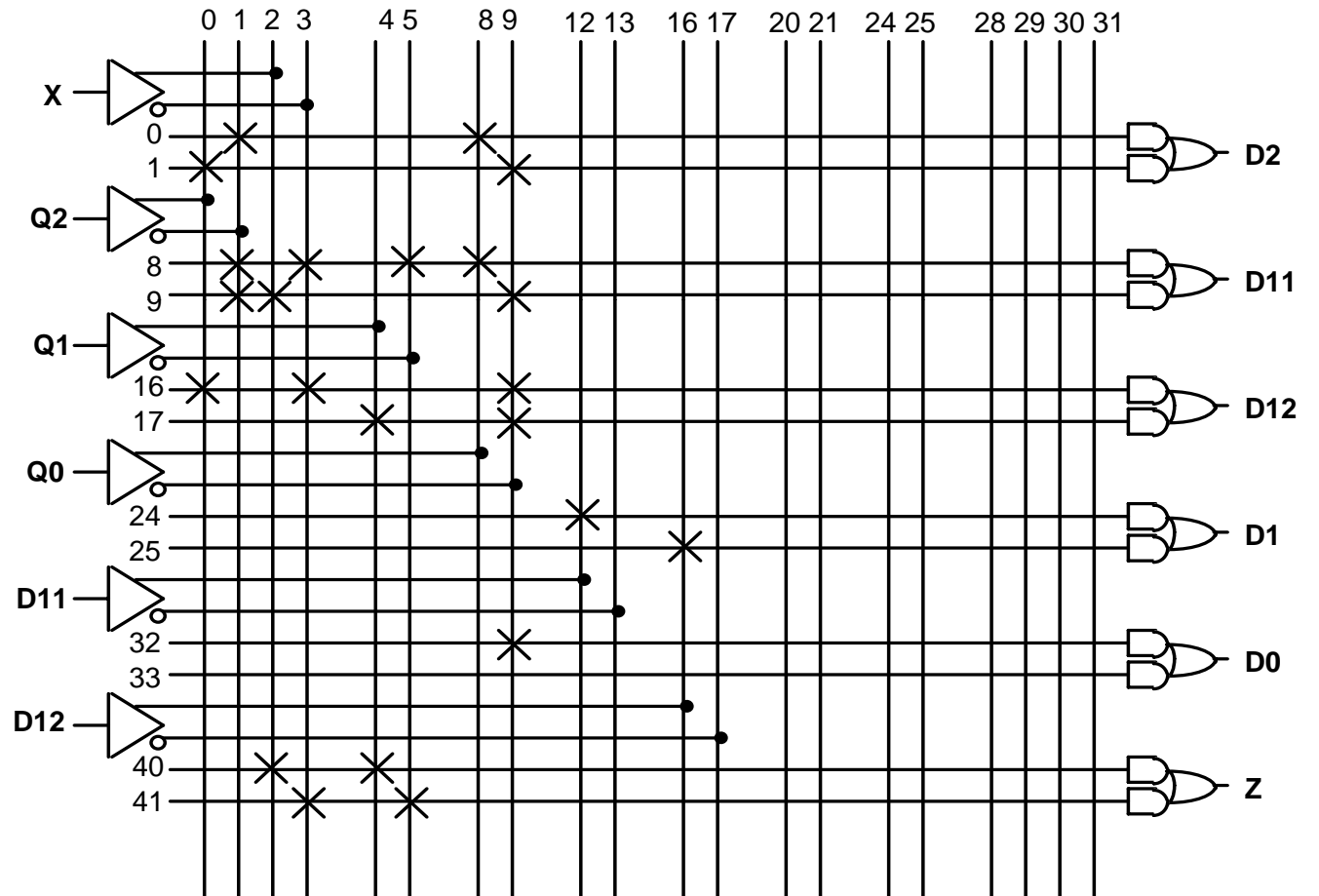 



## *FSM Design with More Sophisticated PLDs*

- Programmable Logic Devices = PLD
  - PALs, PLAs = 10 - 100 Gate Equivalents
- Field Programmable Gate Arrays = FPGAs
  - Altera MAX, FLEX, Stratix Families
  - Actel Programmable Gate Array
  - Xilinx Logical Cell Array
  - 100 – 1,000,000(s) of Gate Equivalents!




## *Case Study: Traffic Light Controller*

- Decomposition into primitive subsystems
- Controller FSM
  - next state/output functions
  - state register
  
- Short time/long time interval counter
- Car Sensor
- Output Decoders and Traffic Lights




# Case Study: Traffic Light Controller

Block Diagram

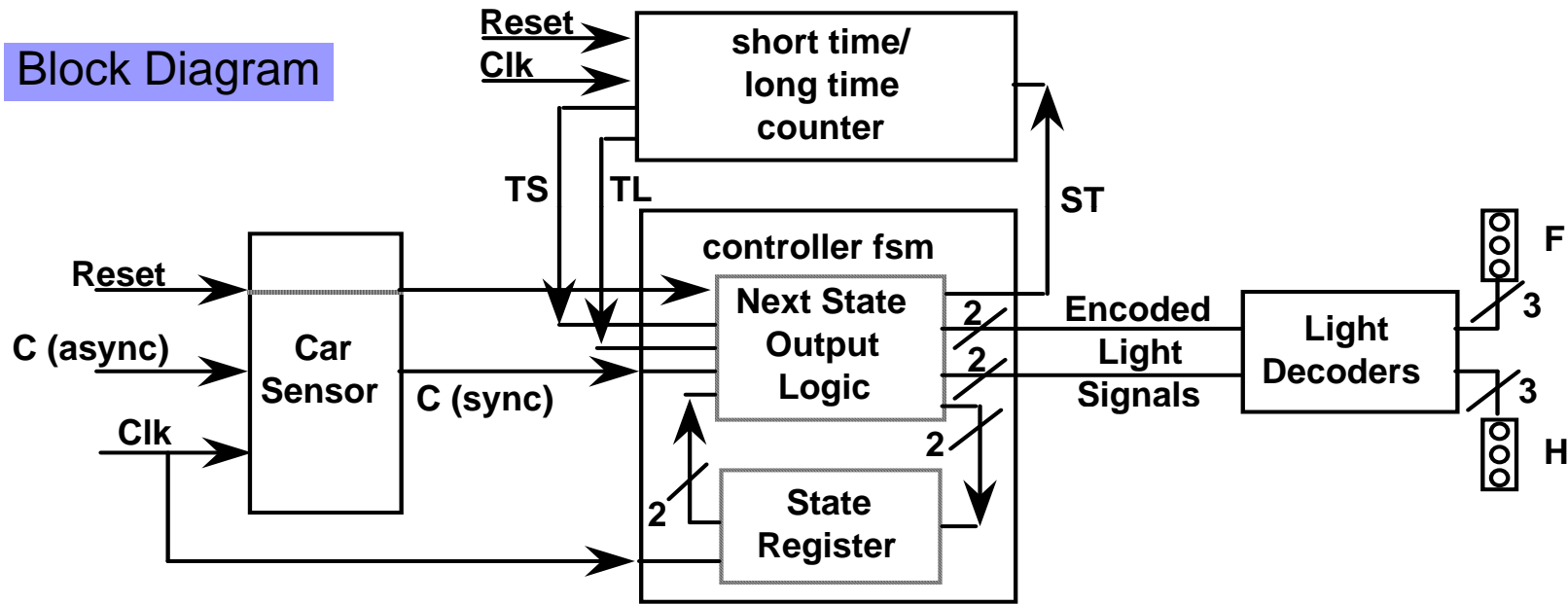


# Case Study: Traffic Light Controller


## Subsystem Logic

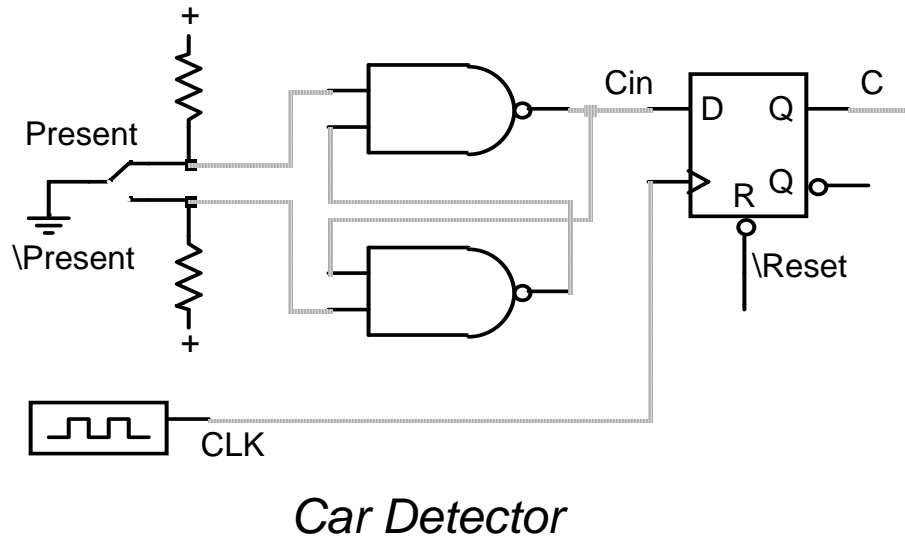

## Light Decoders

 

## Interval Timer

 

# Design Case Study: Traffic Light Controller

## Next State Logic

State Assignment: HG = 00, HY = 10, FG = 01, FY = 11

$$P1 = C TL \overline{Q1} + \overline{TS} Q1 \overline{Q0} + \overline{C} \overline{Q1} Q0 + \overline{TS} Q1 Q0$$

$$P0 = TS Q1 \overline{Q0} + \overline{Q1} Q0 + \overline{TS} Q1 Q0$$

$$ST = C TL \overline{Q1} + \overline{C} \overline{Q1} Q0 + TS Q1 \overline{Q0} + TS Q1 Q0$$

$$HL[1] = TS Q1 Q0 + \overline{Q1} Q0 + \overline{TS} Q1 Q0$$

$$HL[0] = \overline{TS} Q1 \overline{Q0} + TS Q1 \overline{Q0}$$

$$FL[1] = \overline{Q0}$$

$$FL[0] = TS Q1 Q0 + \overline{TS} Q1 Q0$$

PAL/PLA Implementation:

5 inputs, 7 outputs, 8 product terms

PAL 22V10 -- 11 inputs, 10 prog. IOs, 8 to 14 prod terms per OR

ROM Implementation:


32 word by 8-bit ROM (256 bits)

Reset may double ROM size


# Design Case Study: Traffic Light Controller

## Next State Logic

### Counter-based Implementation

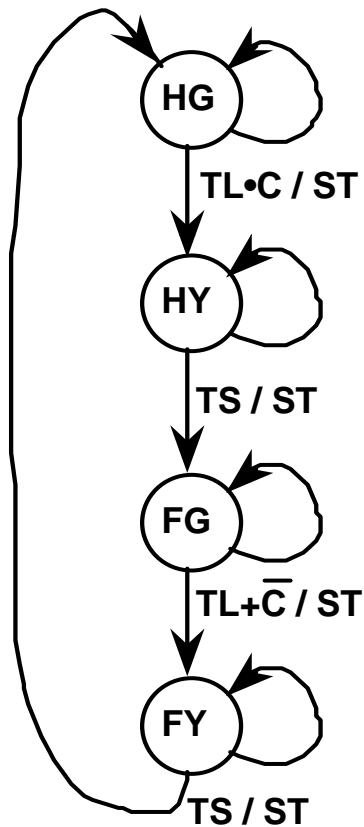

ST = Count

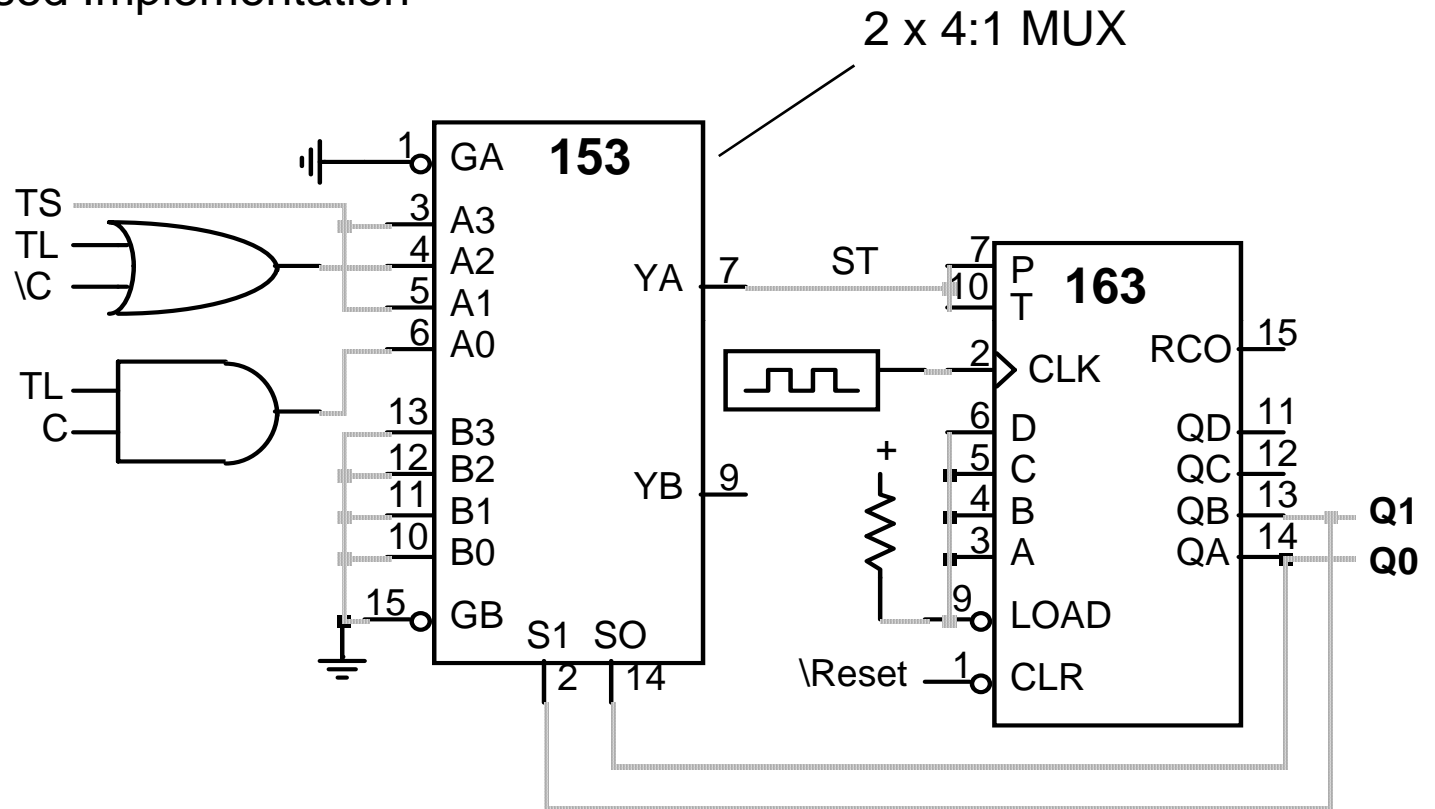

TTL Implementation with MUX and Counter

Can we reduce package count by using an 8:1 MUX?



## *Summary of FSM Implementation*

- Implementation Issues
  - Choice of Flipflops
  - Structured Logic Methods
- ROM based
- PLA/PAL based
- Jump Counter Methods
- Sophisticated PLDs: Altera, Actel, Xilinx